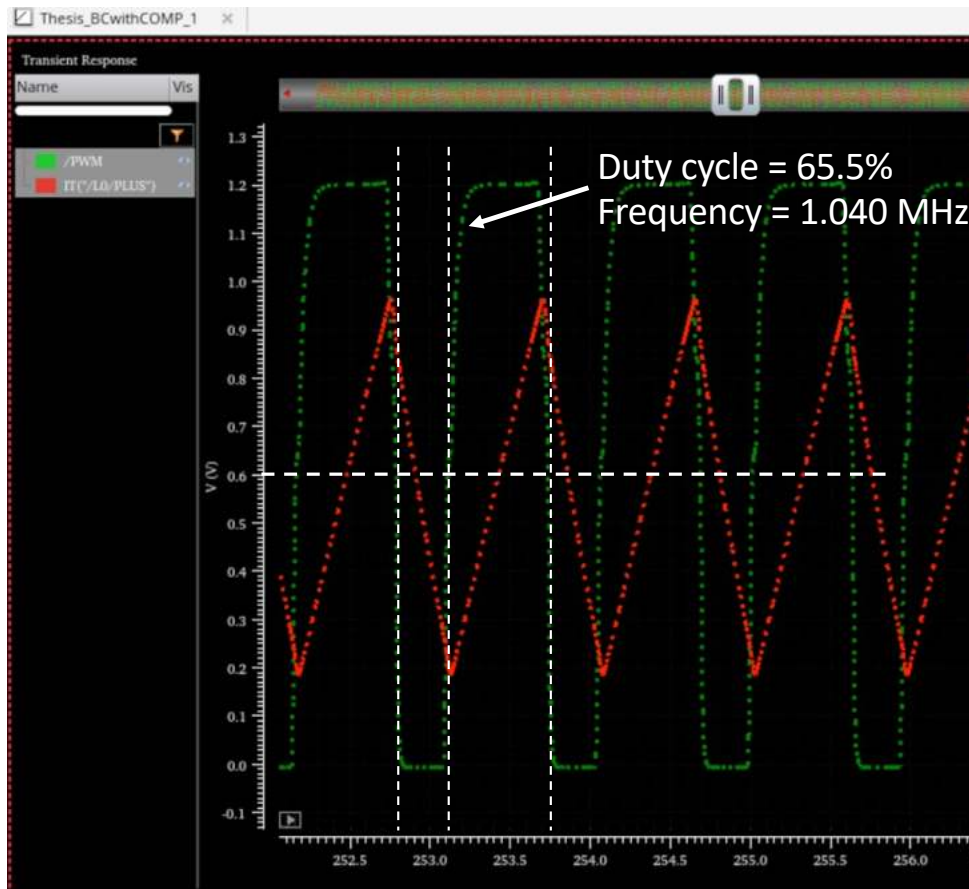



Analysis of Boost Converter Performance Attributes from Data Provided by Mamarts on Cadence Forums^[1]

[1] https://community.cadence.com/cadence_technology_forums/f/custom-ic-design/57450/boost-converter-design-help


Switching Waveform Analysis




Inductor Current Analysis

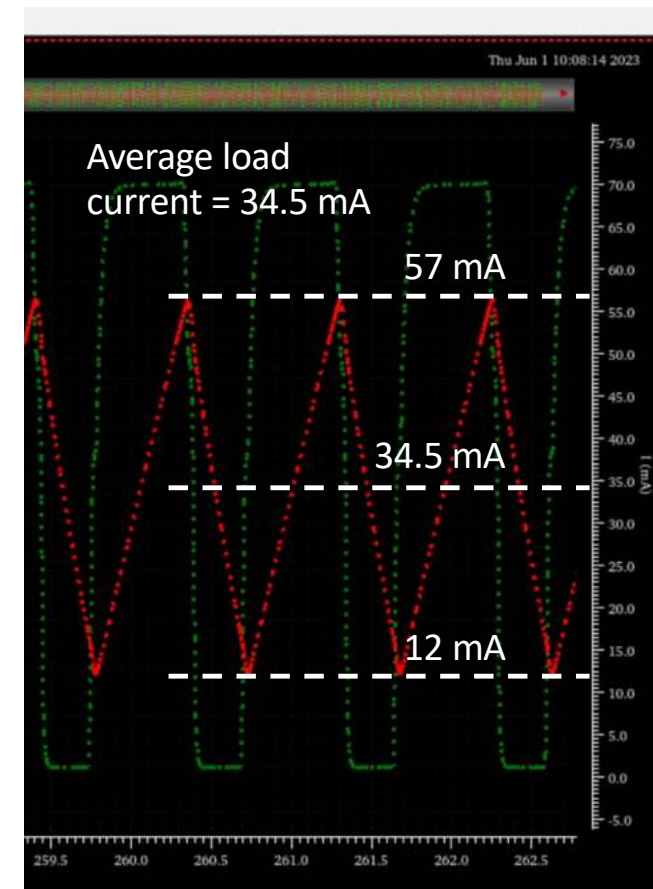

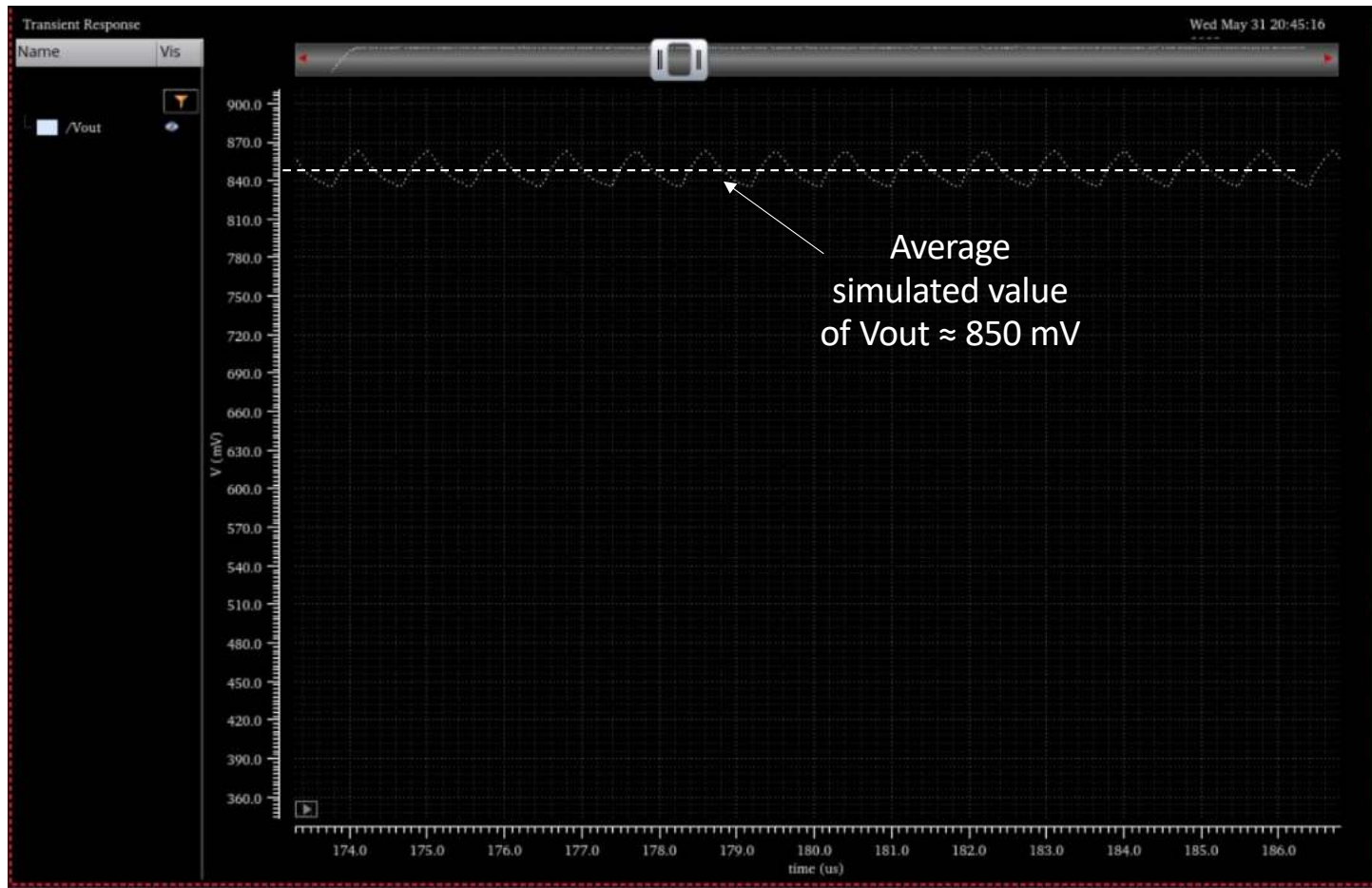Analysis of Boost Converter Simulated Output Voltage Waveform



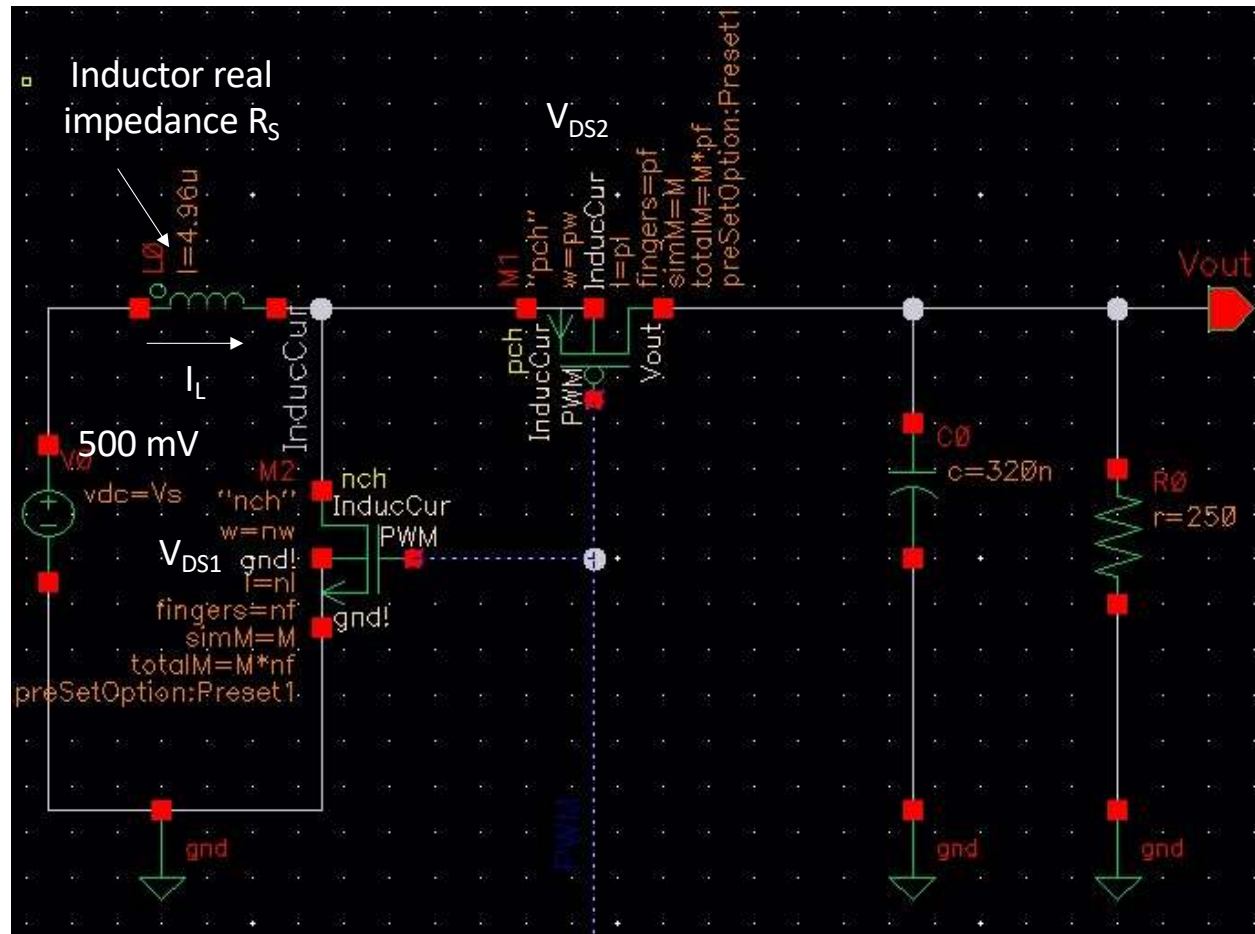Boost Converter Component Values used in Deriving Output Voltage in Continuous Mode of Operation



Expected Boost Converter Output Voltage in Continuous Mode of Operation for Chosen Parameters

$$V_{out} = \frac{V_{in} - I_L R_s}{1 - D_u} - V_{DS2} - V_{DS1} \frac{D_u}{1 - D_u}$$

Equation (1) derived from reference [2]

Case 1:

Your components with my estimates for vds and rs

Parameter	Value	Units
vin	0.5000	Volts
iload	0.0345	A
rs	2.0000	ohms
duty_cycle	0.6550	
vds1	0.1000	Volts
vds2	0.1000	Volts

vout	0.9594	Volts
-------------	---------------	--------------

Value of 959 mV is somewhat close to your measured value of ≈ 850 mV

Case 2:

“ideal” components (vds = 0, rs = 0)

Parameter	Value	Units
vin	0.5000	Volts
iload	0.0345	A
rs	0.0000	ohms
duty_cycle	0.6550	
vds1	0.0000	Volts
vds2	0.0000	Volts

vout	1.4493	Volts
-------------	---------------	--------------

Case 3:

Your components, optimized duty cycle, with my estimates for vds and rs

Parameter	Value	Units
vin	0.5000	Volts
iload	0.0345	A
rs	2.0000	ohms
duty_cycle	0.8680	
vds1	0.1000	Volts
vds2	0.1000	Volts

vout	2.5076	Volts
-------------	---------------	--------------

Increasing duty cycle to 86.8% sets value close to desired value of 2.50 V

On-line Boost Converter Design Example: 0.50 V input/2.50 V output, 37.5 mV Inductor current and 100 mV VDS^[3]

Topology: Boost

Inductance based on the specified minimum load current.

Item	Value	Units
Volts In	0.50	V
Volts Out	2.50	V
Load Current	37.5e-03	A
Freq.	1000	KHz
Vripple	0.025	V
Duty Cycle	84	%
Ipp Inductor	0.00375	A
Ipk Inductor	0.039375	A
Irms	0.035641443573458	A
L	89.6	uH
C	1.26	uF

Duty cycle to of 84% is quite close to computed value of 86.8% on [Page 4](#) to set vout close to desired value of 2.50 V